

# ECE 337 Final Presentation

## Project: Julia Set Fractal Viewer

Lab Section: Friday 11.30a.m

Teaching Assistant: Nicholas Pfister

Team Members
Alan Moreton
Kenji Inoue
Dimitri James
Chongjin Chua

# Overview - Julia Set

What is a Julia Set?


- Fractal
- Subset of Mandelbrot
- Chaotic

What are its functions?

- CGI
- Simulate biological processes, interaction
- Future image compression

Why use an ASIC?

- Faster Calculations

 


1



2


# System Design

2

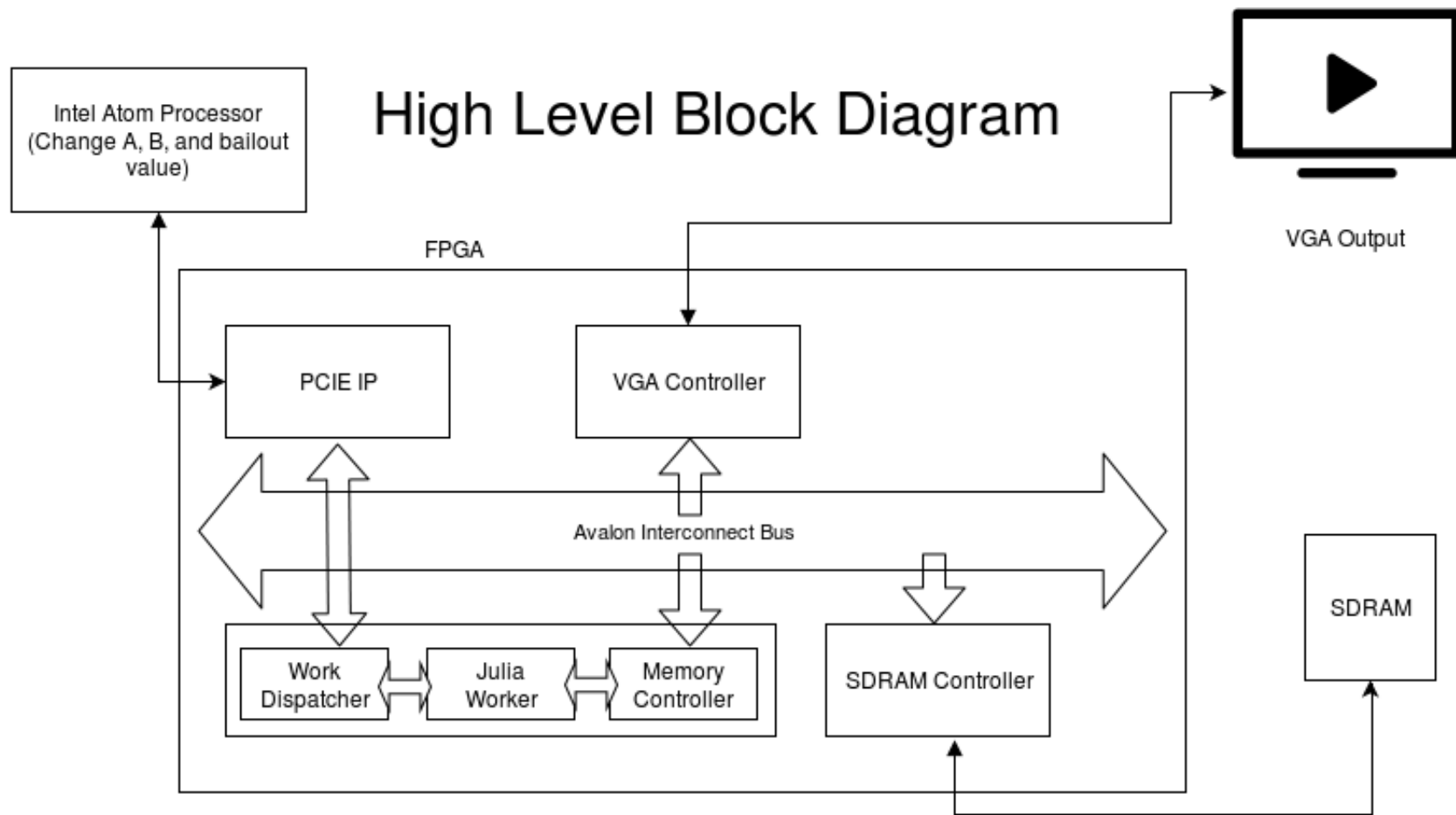

3

# System Design

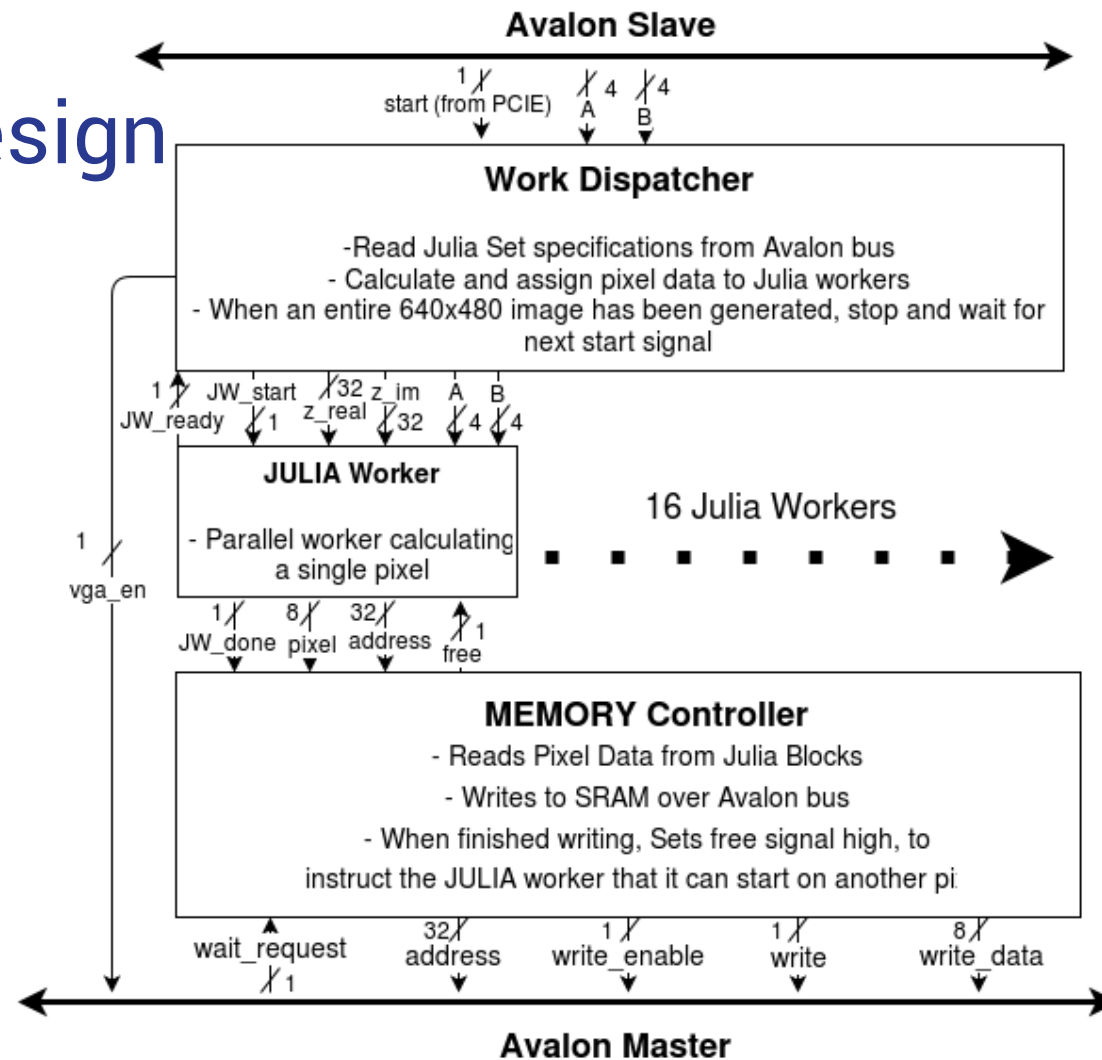

Fixed Criteria	P/F
Test benches exist for all top level components and the entire design. The test benches for the entire design can be demonstrated or documented to cover all of the functional requirements given in the design specific success criteria.	P
Entire design synthesizes completely, without any inferred latches, timing arcs, and, sensitivity list warnings.	P
Source and mapped version of the complete design behave the same for all test cases. The mapped version simulates without timing errors except at time zero.	P&F
A complete IC layout is produced that passes all geometry and connectivity checks.	P
The entire design complies with targets for area, pin count, throughput (if applicable), and clock rate.	P


DSSC	P/F
Calculate a working Julia set block with code that accurately calculates next values and address of memory location	P
Dispatcher correctly assigns work to workers that are available	P
Memory controller correctly assigns calculated values to memory	P
Julia set updates the display with the new zoomed image manually	F
Successfully integrate FPGA and Avalon Bus Interface	P&F
Different patterns using coefficients	P
Vga controller successfully read data from SDRAM and display data on screen	P

# Results (julia worker)

## DSSC 1

Julia set algorithm:  
 $Z_{\text{new}} = (Z_{\text{old}})^2 + C$

6

 

Red line: The positive clock edge where valid color and address are passed to Memory Controller.

Blue circle: Number of iterations = 255, Color = 00000000 (black)

Address = 0852d100 ( x = 384, y = 264 )


6

# Results (julia worker)

## DSSC 1

Julia set algorithm:  
 $Z_{\text{new}} = (Z_{\text{old}})^2 + C$

7

 

Red line: The positive clock edge where valid color and address are passed to Memory Controller.

Blue circle: Number of iterations = 5, Color = 00FF0000 (red)

Address = 081f5900 ( x = 100, y = 100 )


7


 
## Results (dispatcher) DSSC 2


Red line: Shows dispatcher assigning jobs to workers as they are available and de-asserting the “done flag”

Blue circle: Shows dispatcher logic taking effect as jobs become more complicated






 Blue: Pixel and address data  
muxed from concatenated line.



# Results (custom\_master\_slave)

10

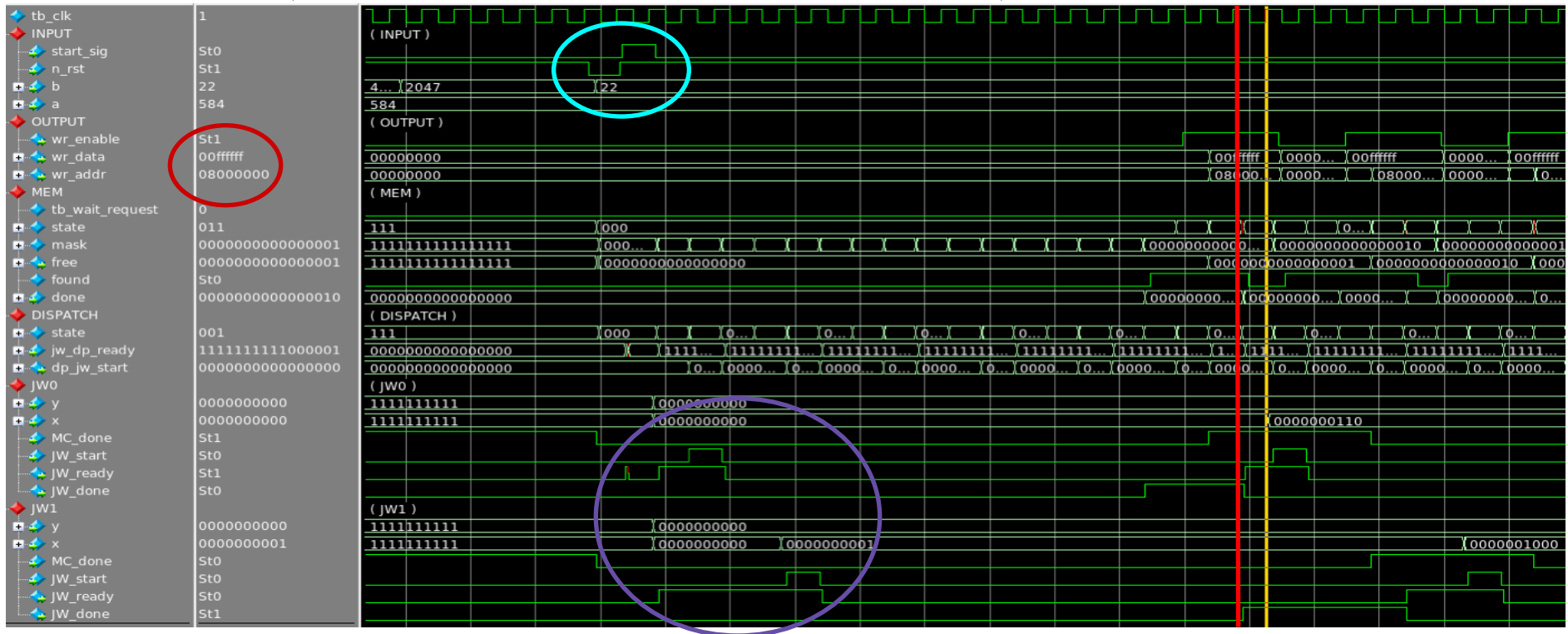

Blue circle: Custom logic reset followed by start signal


Purple circle: Julia Workers asking for task/assigned with task

Red circle: Output (Address = 08000000, Color = 00FFFFFF)

10

# Results (custom\_master\_slave)

11

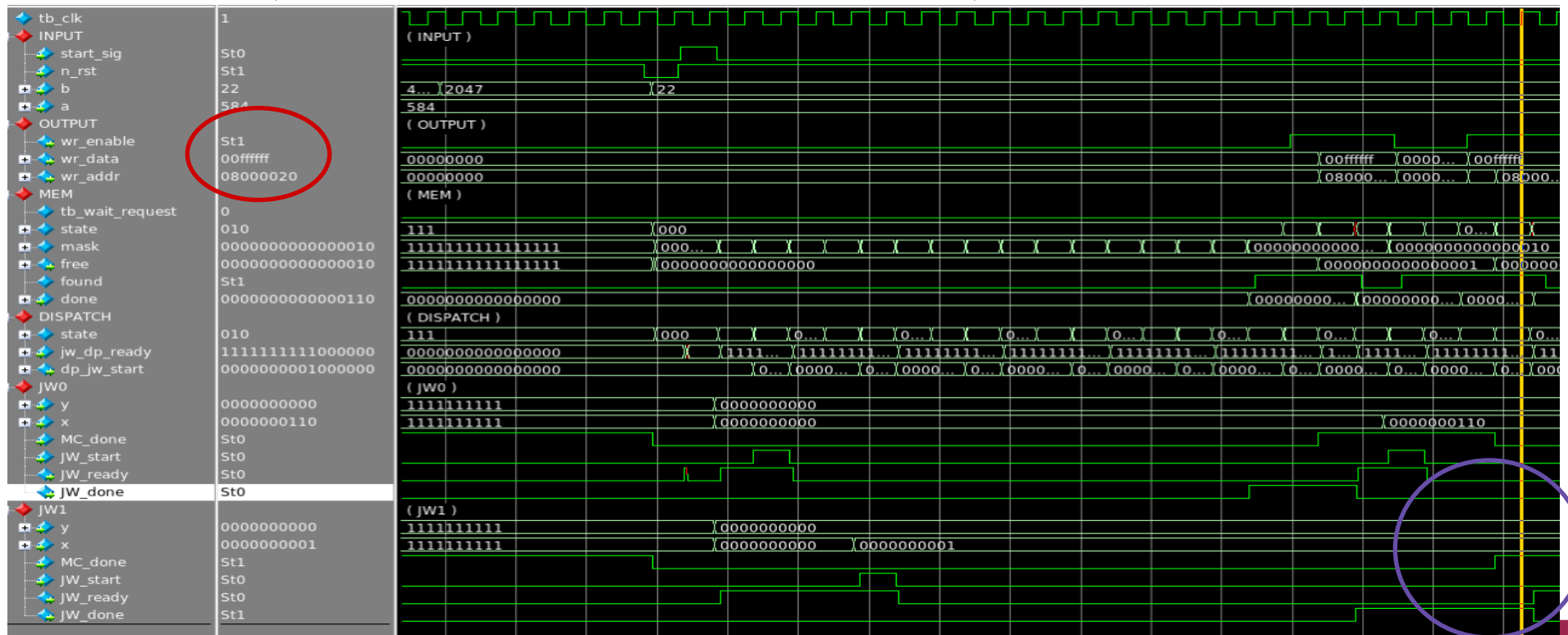

Purple circle: JW1 write to SDRAM after JW0 is done writing

Red circle: Output (Address = **08000020** , Color = 00FFFFFF)

11


# Conclusions

1. The biggest challenges in doing this design:
  - a. FPGA integration
  - b. Understanding how the Avalon bus system works.
  - c. Writing data to SDRAM on the FPGA
2. How we would approach our design differently if we had to do it over again:
  - a. Use a more efficient round robin approach
  - b. More Julia Workers
3. What improvements we would make given more time:

Questions?

# Results (julia worker) [BACKUP SLIDE]

## DSSC 1

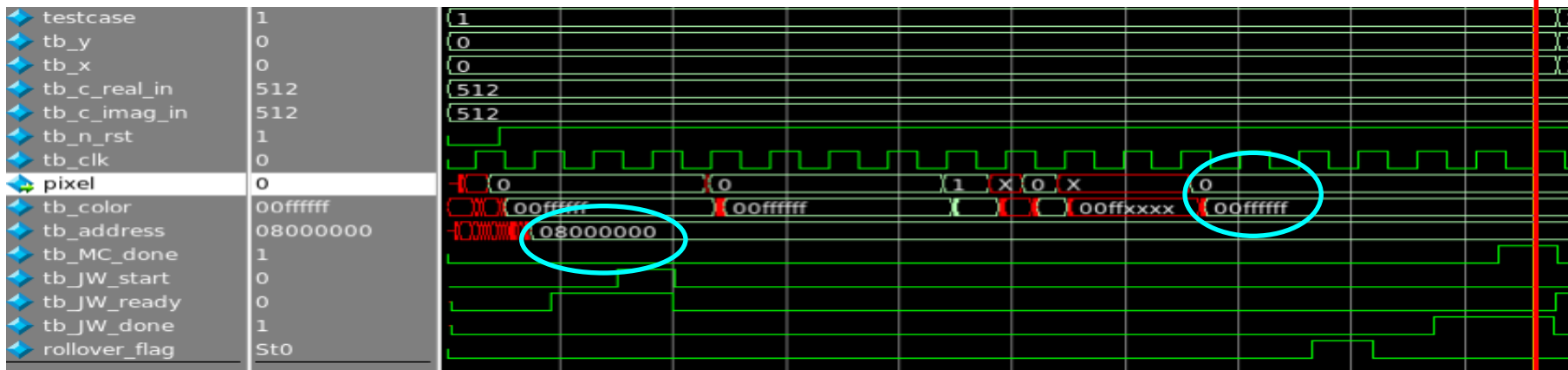


Red line: The positive clock edge where valid color and address are passed to Memory Controller.

Blue circle: Number of iterations = 0, Color = 00FFFFFF (white)

Address = 08000000 ( x = 0, y = 0 )

# Results (Julia Worker)[BACKUP SLIDE]

## DSSC 1

 

Fundamental block in each Julia Workers


Executes fixed point multiplication

Julia Set algorithm:  $Z_{new} = Z_{old}^2 + \text{Constant}$

Metastable state will propagate to other part of the design




# Layout

 


Synthesis Critical Path Delay : 3.5ns  
(from Memory Controller state register  
to master address)

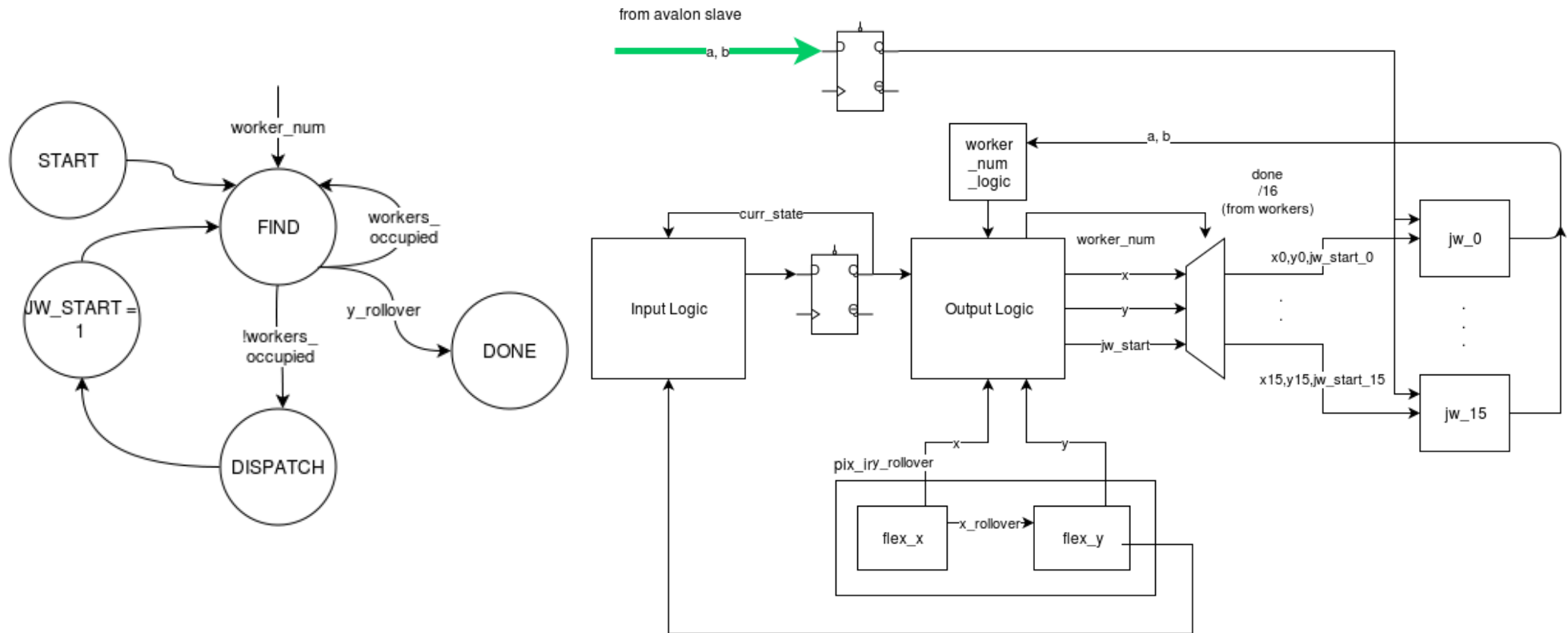
# Work Dispatcher - Architecture and Logic




# Julia Worker - Architecture

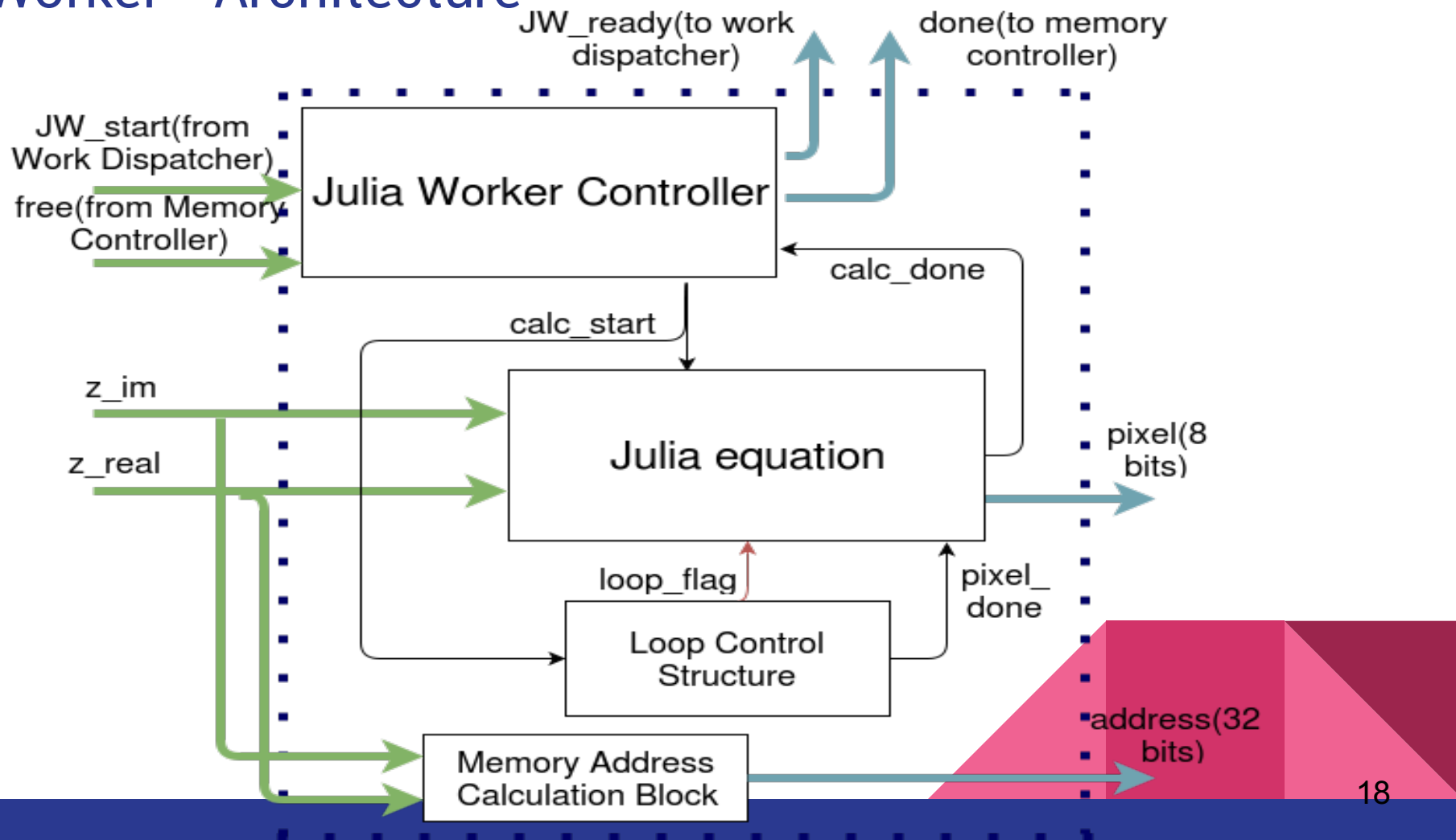


# Julia Worker - Logic

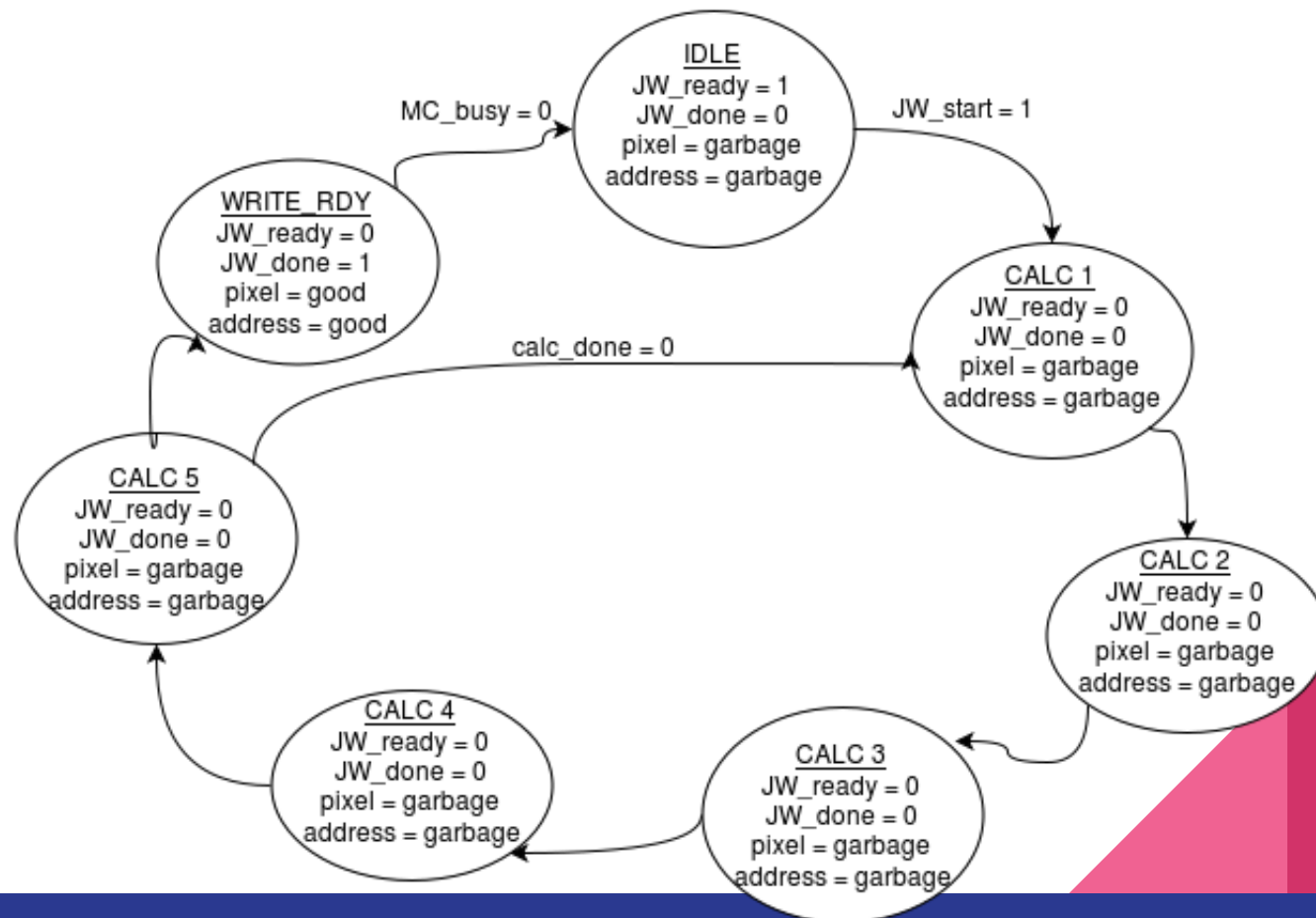


## Julia Worker - Julia Equation

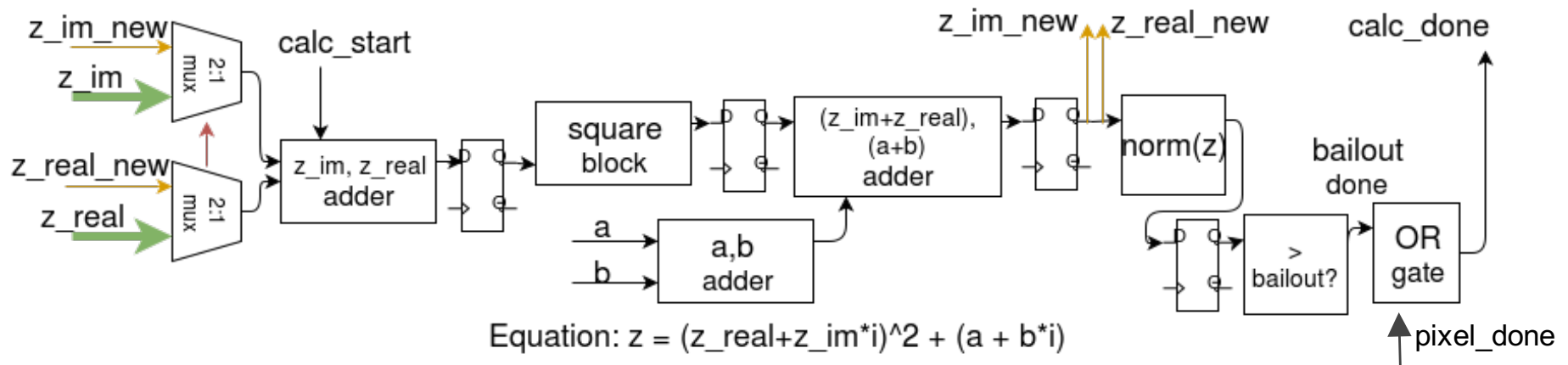

## Julia Worker - Loop Control Structure

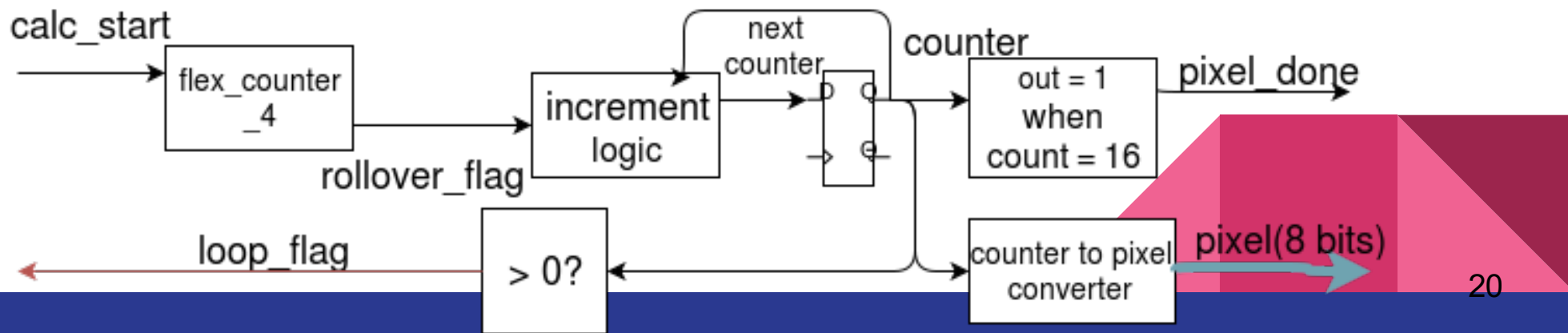

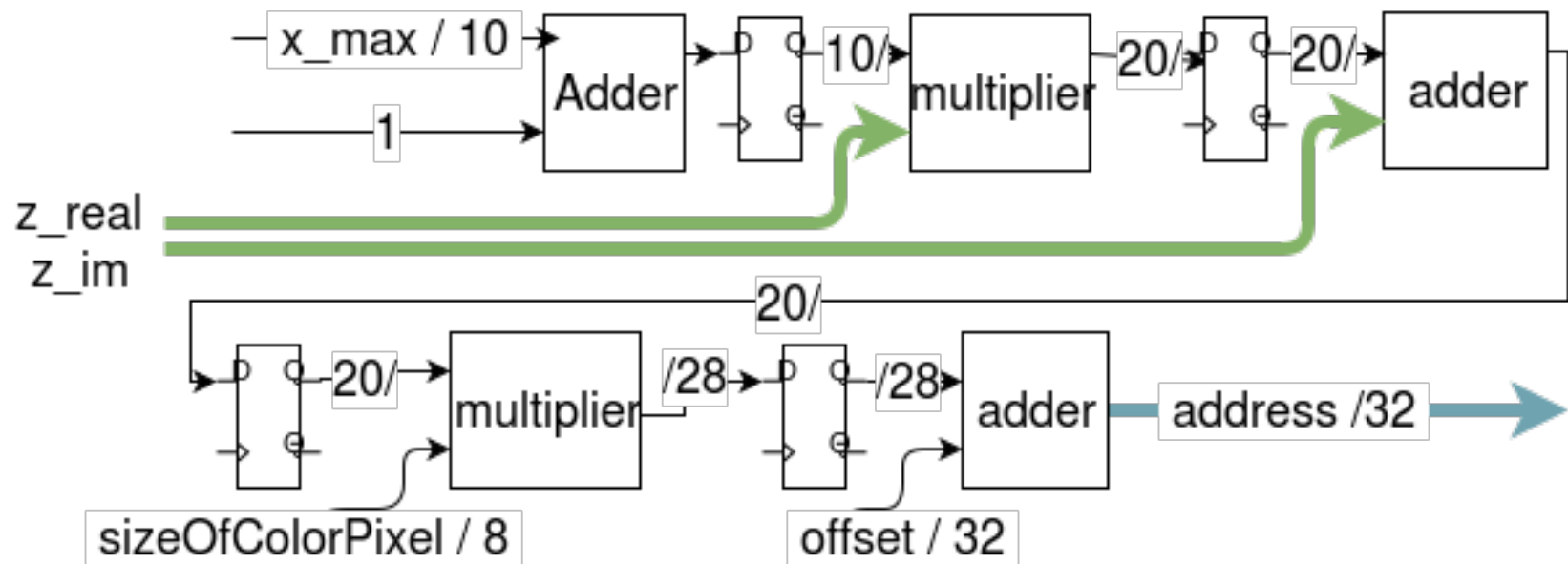
## Julia Worker - Memory Address Calculation Block




Equation:  $(\text{sizeofColorPixel} * ((x_{\text{max}} + 1) * y) + x) + \text{offset} = \text{address of start of pixel}$

# Memory Controller - Flow

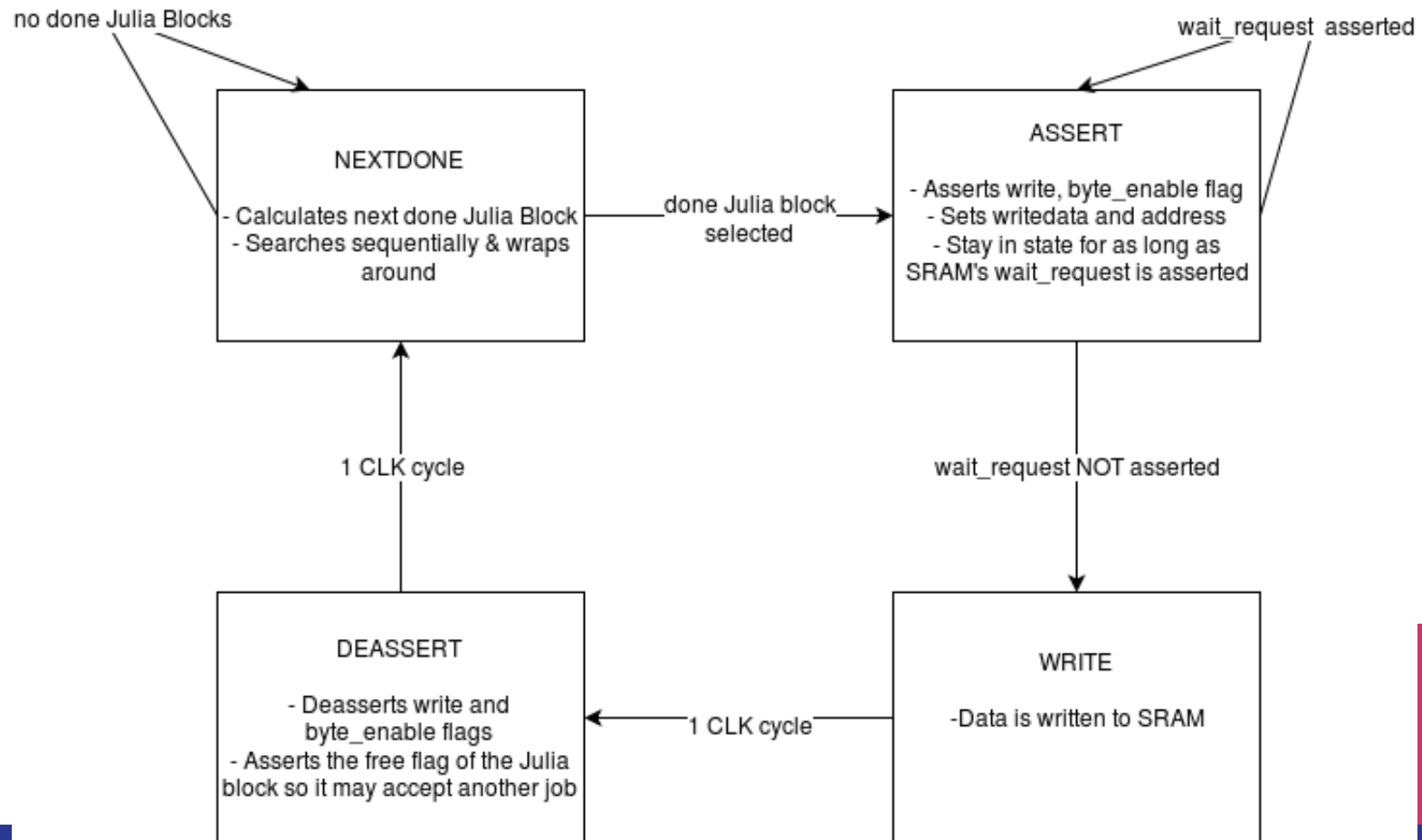




# Memory Controller - Architecture

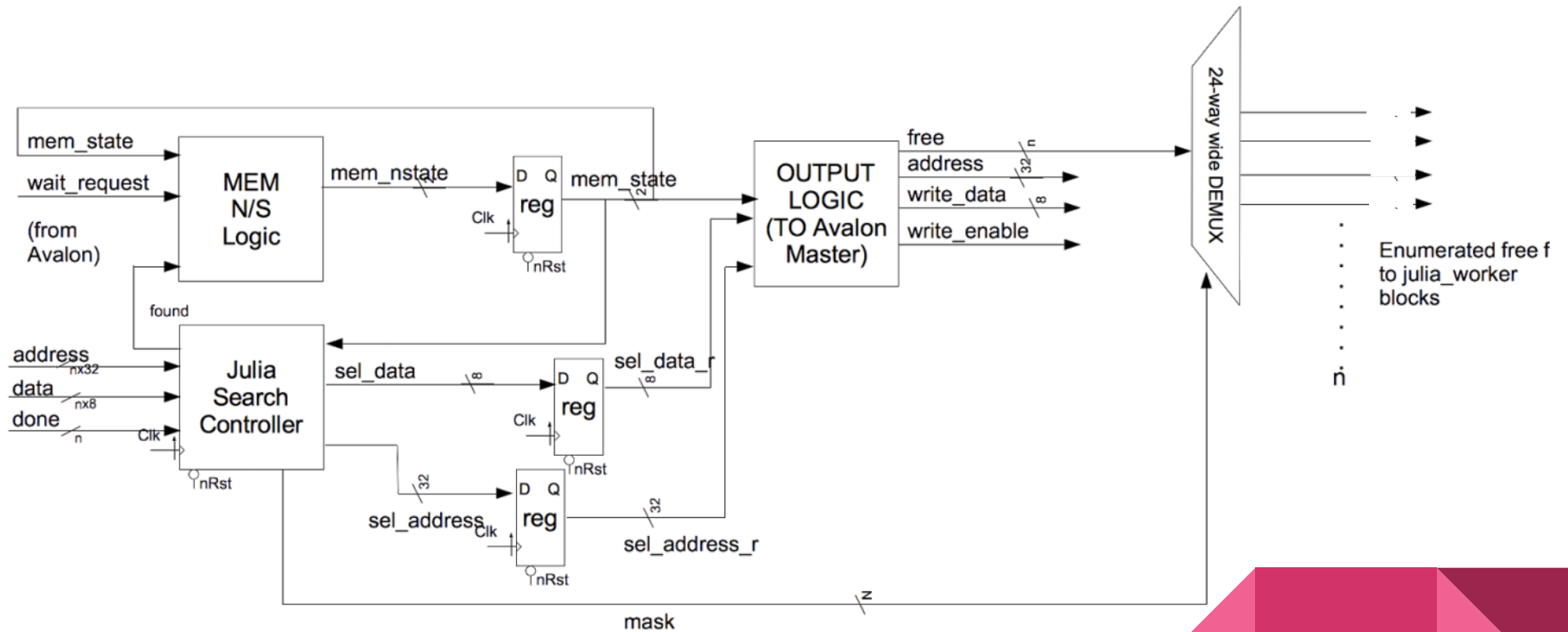
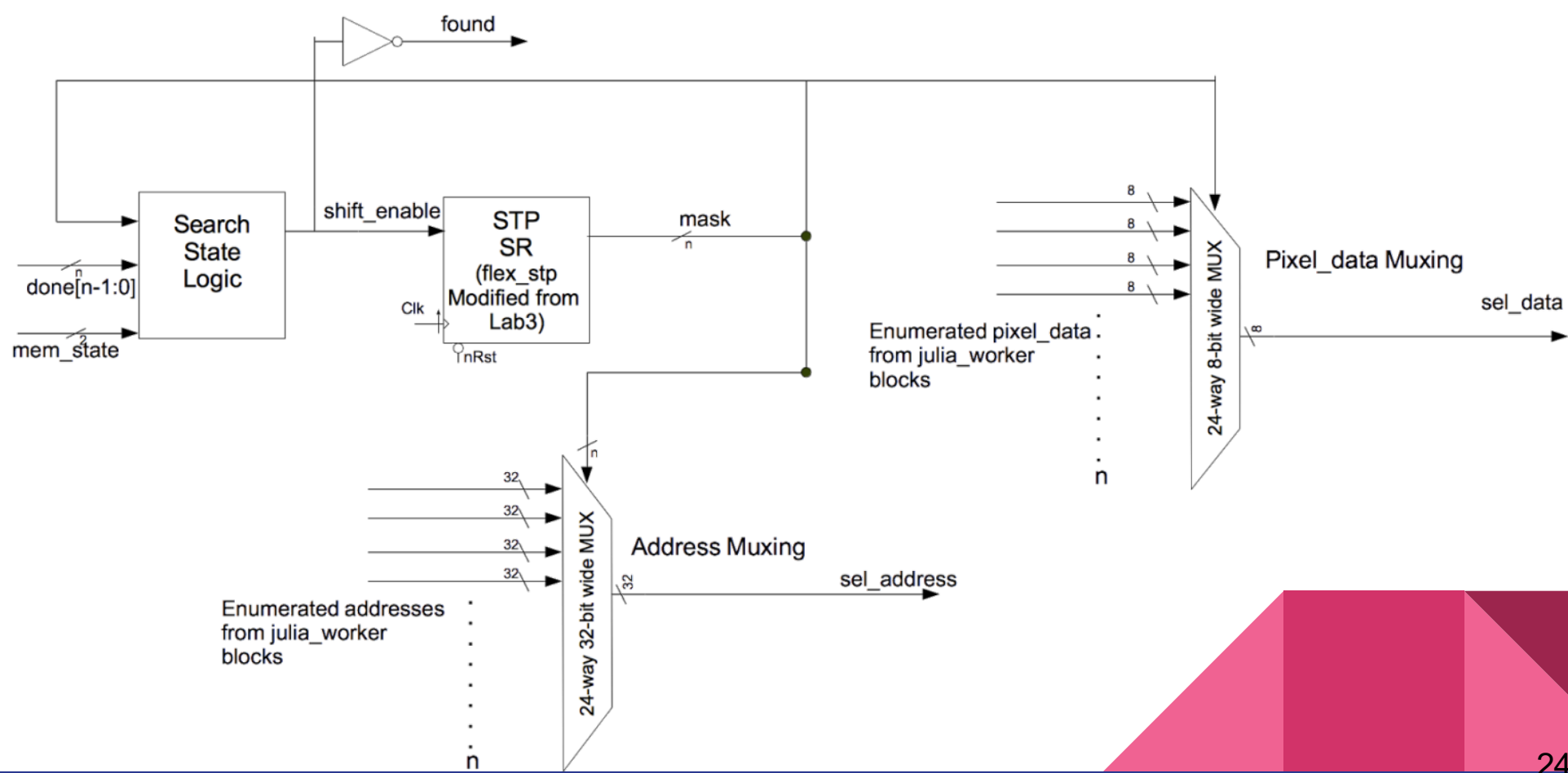
# Memory Controller - Julia Search Controller Block



# Area Budget

Core Area Calculations								
Name of Block	Category	Gate/FF Count	Area (um2)	Comments	Total:			
Input/Output	Reg. w/ Reset	3	7,200	State Machine	9x9 multipliers:	560	pixel address calculator	
Worker_num_logic	Combinational	54	40,500	Worker selector block	18x18 multipliers	360	julia worker	
Flex_x	Combinational	57	42,750	X incrementer	embedded multipl	360	Memory Controller	
Flex_y	Combinational	57	42,750	Y incrementer			Dispatcher	
Worker_select_mux	Combinational	256	192,000	Outputs values to the worker				
z real, z im adder	Combinational	20	15,000	4 bits ripple carry adder				
a, b adder	Combinational	20	15,000	4 bits ripple carry adder				
(z real + z im), (a+b) adder	Combinational	40	30,000	8 bits ripple carry adder				
z real, z im square	Combinational	1	434,214					
normalize z	Combinational	4	22,248	2 multipliers, 1 adder, 1 sqrt				
bailout and z comparator	Combinational	11	8,250	8 bits comparator				
pixel incrementer	Combinational	20	15,000					
pixel val register	Reg. w/ Reset	4	9,600	4 flip-flops				
pixel val output logic	Combinational	5	3,750	4 bits comparator				
4:3 encoder	Combinational	7	5,250					
z flip_flop	Reg. w/ Reset	8	19,200	8 flip-flops				
2:1 multiplexer	Combinational	32	24,000	8 x 2:1 mux, each mux has 4 gates				
Adder	Combinational	3	102,816					
Multiplier	Combinational	2	868,428					
Memory Controller State Reg	Reg. w/ Reset	2	4,800	Assume 4 states				
Address data reg	Reg. w/ Reset	32	76,800	32 bit				
Pixel data reg	Reg. w/ reset	8	19,200	8 bit				
Shift register	Reg. w/ reset	4	9,600					
Pixel Data Mux (16 to 1)	Combinational	128	96,000	for n-julia workers				
Free Demux (1 to 16)	Combinational	128	96,000	for n-julia works				
Next State Logic	Combinational	4	3,000					
Search Logic	Combinational	4	3,000	"current state logic"				
Output logic	Combinational	4	3,000					
Total Core Area			2,209,356					

# Timing Budget

Starting Component	Propagation Delay (ns)	Combinational Logic	Propagation Delay (ns)	Ending Component	Setup Time or Propagation Delay (ns)	Total Path Delay (ns)	Target Clock Period (ns)		
Julia Worker Register	0.1	Julia Worker Output logic, flex_counter_4, increment logic	127.3	Counter Register	0.1	127.5	1000		
Normalize Register	0.1	Bailout Check, OR Gate, Julia Worker Next State Logic	89.5	Julia Worker Register	0.1	89.7	1000		pixel address calculator
Counter Register	0.1	Counter Comparator, OR Gate, Julia Worker Next State Logic	65.5	Julia Worker Register		65.6	1000		julia worker
Initial Register	0.1	$((x\_max+1*y)+x)*sizeOfColor$ + mem offset adder	81.27	Output Register	0.1	81.47	1000		Memory Controller
mem_state register	0.1	memory controller output logic, demux, julia worker next state logic	74.5	Julia Worker Register	0.1	74.7	1000		Dispatcher
*J.W = Julia Worker									

# Data Sheet and Documentation

VGA chip data sheet

<http://www.analog.com/media/en/technical-documentation/data-sheets/ADV7123.pdf>

Avalon reference manual

[https://www.altera.com/content/dam/altera-www/global/en\\_US/pdfs/literature/manual/mnl\\_avalon\\_spec.pdf](https://www.altera.com/content/dam/altera-www/global/en_US/pdfs/literature/manual/mnl_avalon_spec.pdf)

PCIe

<https://sites.google.com/site/de2i150atpurdue/how-to-write-the-software>

<https://sites.google.com/site/de2i150atpurdue/designing-your-own>

DE2i-150 FPGA System User Manual download link